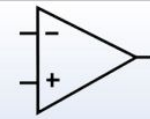


Operational Amplifiers



The operational amplifier (op amp)


A device for nearly ideal DC amplification. Used to perform mathematical operations such as adding, subtracting, integration and differentiation.

Terminology

Inverting input

Output

Non-inverting input

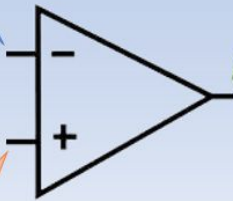


In a DC (steady state) circuit, op amps

1. Has no current flowing on the **inverting input**
2. Has no current flowing on the **non-inverting input**
3. Has no current flowing on the **output**
4. The voltage between the inputs is 0

Assignment

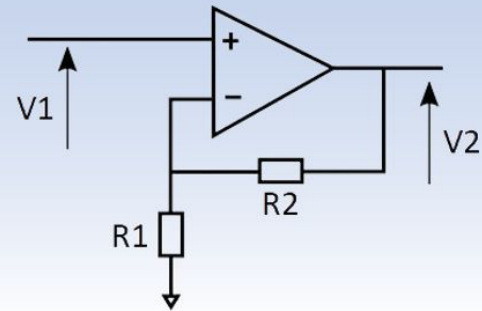
- a) Show that the gain A of the circuit is $A = \frac{V_2}{V_1} = 1 + \frac{R_2}{R_1}$!
- b) Why is it called a non-inverting circuit?




Example

Replacing an op amp with simple electric components


Step 0: Draw the circuit!

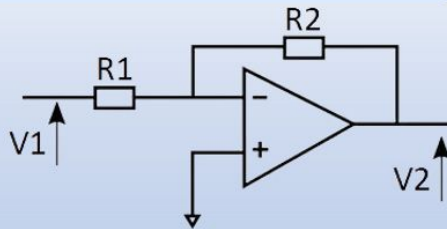


Step 1: Cut the output!

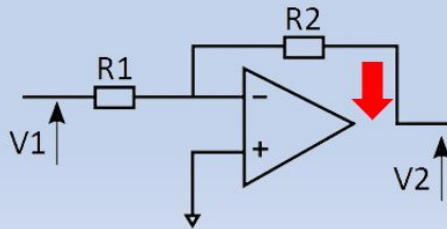

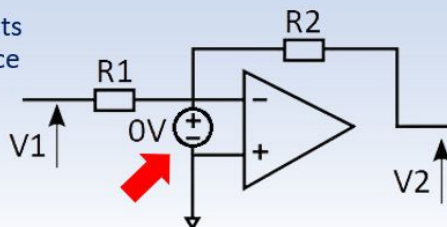
Step 2: Connect the inputs with a voltage source of 0V!



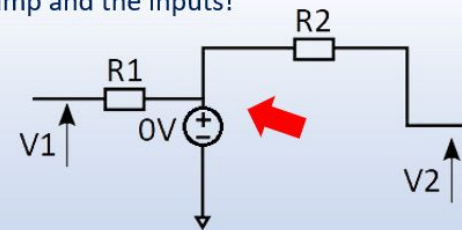Step 3: Delete the op amp and the inputs!



Step 4: Reorganize the circuit!

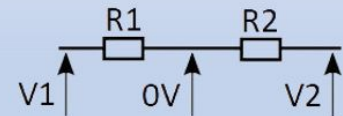

Step 5: Solve the circuit!

We can see that the current passing through R_1 and R_2 is identical. Using Ohm's law:

$$V_1 - 0 = V_1 = IR_1$$

$$0 - V_2 = -V_2 = IR_2$$

$$A = \frac{V_2}{V_1} = \frac{-IR_2}{IR_1} = -\frac{R_2}{R_1}$$